

Scheme – E

Sample Question Paper

Course Name : Computer Engineering Group

Course Code : CO/CM/IF/CD

Semester : Third

Subject Title : Digital Techniques

Marks : 100

12064

Time: 3 Hours

Instructions: 1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Use of non-programmable calculator is permissible.

Q.1 Attempt any TEN of the following:

(10 x 2 = 20)

- a) Define Resolution, Linearity of ADC.
- b) Define Fan-out & Figure of merit.
- c) Convert the following Hex number to binary number i) 3FE4 H ii) 19BA H
- d) Find out the 2's complement of following numbers i) 1101 ii) 10110
- e) Draw logic symbol & truth-table for NAND gate.
- f) Perform binary subtraction of following numbers $(10110)_2 - (01101)_2$
- g) Explain positive and negative logic in TTL.
- h) Draw truth table for Half adder and logic diagram.
- i) Why flip-flop is called as a basic memory cell.
- j) Give the classification of different types of semiconductor memories.
- k) Draw the symbol and truth table for T & D flip-flop.
- l) State two advantages of digital circuits.

Q.2 Attempt any FOUR of the following:

(4 x 4 = 16)

- a) Perform BCD addition for the following-
 - i) $(25)_{10} + (36)_{10}$
 - ii) $(99)_{10} + (11)_{10}$
- b) Perform subtraction using 2's complement-
 - i) $(0101)_2 - (1000)_2$
 - ii) $(100011)_2 - (100101)_2$

- c) For the following decimal numbers convert these to Octal no. and Hex nos.
 i) 1024 ii) 66
- d) Why NAND gate is called Universal gate? Implement XOR gate using only NAND gate.
- e) Prove the following logic expression using Boolean algebra

$$AB + CD = (A + C)(A + D)(B + C)(B + D)$$
- f) State and prove the De-Morgans theorem

Q.3 Attempt any FOUR of the following: (4 x 4 = 16)

- a) Simplify following using K-map & realize using AND, OR, NOT.

$$(A, B, C, D) = \sum m(1, 3, 7, 8, 10, 12, 13, 15)$$
- b) Implement the following function using 16:1 MUX.

$$Y = \sum m(K1, 2, 5, 6, 8, 12)$$
- c) Explain BCD to seven-segment decoder.
- d) Draw block diagram of a 2 bit digital comparator accepts 2 words
 $A = a_2 a_1$ and $B = b_2 b_1$ and gives three outputs G, E and L.
 i) The output G is high when $A > B$
 ii) The output E is high when $A = B$
 iii) The output L is high when $A < B$
- e) Convert the following Boolean functions into standard SOP form.
 i) $A + B + C$
 ii) $AB + CD + AD$
- f) Describe the ALU 74181 with a neat diagram

Q.4 Attempt any FOUR of the following: (4 x 4 = 16)

- a) Design MOD 5 asynchronous counter.
- b) What is race around condition? How is it eliminated using Master-slave JK flip-flop.
- c) Describe the function of 4-bit SISO shift register with the help of block diagram, truth-table, timing diagram.
- d) Differentiate Synchronous & Asynchronous Counter (any four points).
- e) Draw neat diagram of clocked SR flip-flop using NAND gates and write its truth table.
- f) Explain 3-bit UP ripple (Asynchronous) counter.

Q.5 Attempt any FOUR of the following:


(4 x 4 = 16)

- a) Differentiate between static & dynamic RAM.
- b) Draw neat diagram of R/2R ladder type DAC. Find its output expression.
- c) Write a short note on EEPROM.
- d) Compare volatile and non-volatile memory.
- e) The LSB of 3bit DAC represent 0.2 V What value of voltage will be represented by following binary words
i) 011 ii) 110
- f) Draw the diagram of Successive approximation ADC and describe its operation

Q.6 Attempt any FOUR of the following:

(4 x 4 = 16)

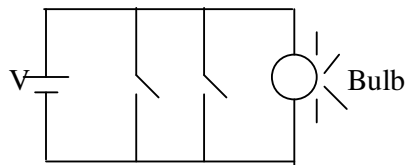- a) Solve POS expression using K-map
i) $F(A, B, C, D) = \prod M(2, 8, 9, 10, 11, 12, 14)$
- b) For the circuit shown below write the truth table.



- c) Determine the frequency at the output of last (MSB) flip – flop for an input clock frequency of 2 MHz.
- d) Explain the specifications of DAC (any four).
- e) Write the advantages & disadvantages of dynamic RAM.
- f) Explain Full Subtractor using its truth table and logic diagram.